
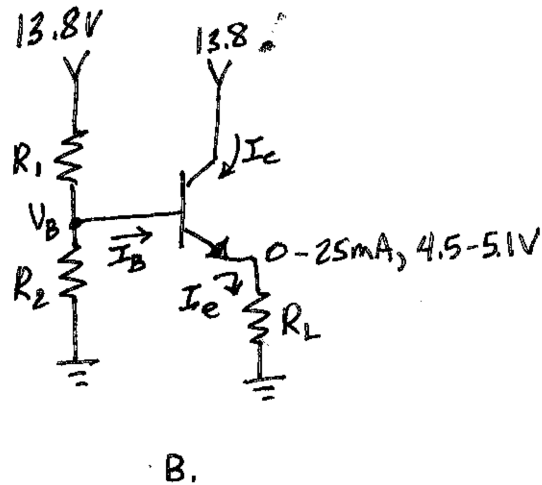


Let's explore two DC power supply designs. Suppose you have a 12V car battery (so its voltage is typically 13.8VDC) and you want to power some digital logic circuits that require 4.5-5.1VDC at 0-25mA. How do you do that? Exceeding 5.1V will blow up the logic circuits and below 4.5V they stop working reliably. Let's compare two designs: a passive voltage divider (A) and a 1-transistor power supply (B).

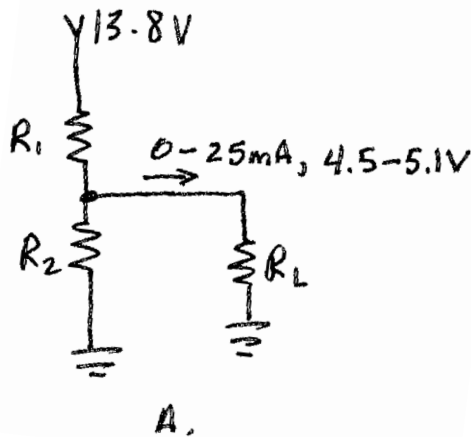

- 1) Show that the digital circuits are equivalent (*from the point of view of the power supply*) to a load impedance $> 180 \text{ Ohms}$.
- 2) Design a voltage divider circuit with 2 resistors as your power supply (drawing A). Show that their values are around 38 and 65 ohms. (Hint: you'll need 3 equations relating the 3 unknowns. One equation is $R_L = 180\Omega$ or ∞ . You get multiple equations for R_1 and R_2 by analyzing the circuit under different extremes, like no load and maximum load).
- 3) Show that this power supply draws $\sim 1.8\text{W}$ of power with no load and 2W under full load. Show that its *efficiency* (power to load / total power used) is $\sim 5\%$.
- 4) Now build an equivalent power supply with an emitter follower (drawing B). Assume $V_{BE} = 0.6\text{V}$, $h_{fe} = 100$. Label all voltages and currents (more variables, more equations) under the two extreme values of $R_L = 180\Omega$ and ∞ . Show the effective impedance the voltage divider sees "looking at" the base at full load is $\sim 20\text{k}\Omega$.
- 5) Show the voltage divider resistors should be $4\text{k}\Omega$ and $5.8\text{k}\Omega$.
- 6) Show this power supply uses $\sim 19\text{mW}$ without load
- 7) Under full load, show the transistor dissipates $\sim 230\text{mW}$ (from the collector to emitter), and the efficiency of the fully loaded power supply is $\sim 30\%$, five times better than the passive one. Remember, from the point of view of R_L , these two power supplies behave the same. But the transistor supply runs vastly cooler, delivering the same power to the load with much less waste.
- 8) What key lessons did you learn from this exercise?