

Exploring Arduino Analog Input Resistance


16 Feb 2023

B. Rasnow

Objective: Better understand the DC input resistance of the Arduino Nano analog inputs. My goal is not to quantify the inputs like a Thevenin equivalent circuit¹, but much more simply, to determine ranges of values of series resistors ($R3$ in Fig. 1) that might protect the Arduino from excessive voltage while not introducing errors in the values that are measured.

Methods:

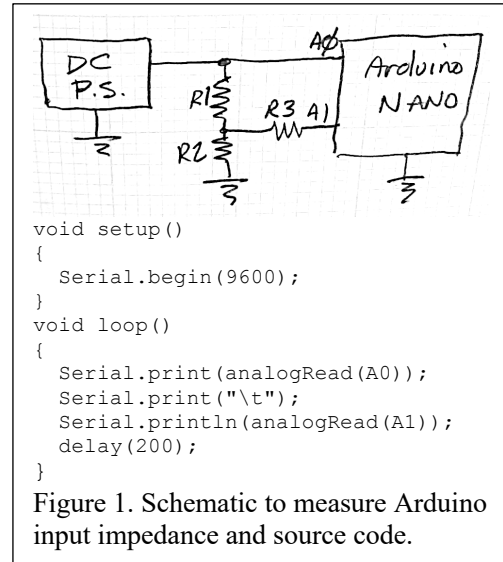- 1) Documentation – google it.
- 2) Measure it – measure analog voltages through voltage dividers and series resistors. The circuit in Fig. 1 was used. The DC power supply (LM317) was set to $\sim 2.5V$ and not adjusted during the experiment (to ensure not exceeding a safe 5V). A0 was sometimes switched to ground and the power supply V_{out} . The Arduino was programmed with the following code, modified from File \rightarrow Examples \rightarrow AnalogReadSerial (Fig. 1)



Results:

- 1) Documentation: Searching “arduino analog input impedance”, I found a rich discussion at: <https://forum.arduino.cc/index.php?topic=65134.0>²: “The ATmega328P datasheet has this info way in the back: Table 28-16 (page 328). The analog input resistance is claimed to be 100 Mohms. During an actual sample, the input resistance is temporarily a lot lower as the sampling capacitor is charged up so it is recommended that whatever you connect to the A/D have an output impedance of 10k or less for best accuracy.” And “the sample/hold cap has only 6us in which to charge and settle in normal operation, fortunately its very small (14pF)”. They recommend adding an external 0.1uf cap when measuring DC voltages.
- 2) Measurements:
 - a) With $R1=R2=R3 = 10k$ and $V_{in} \sim 2.5V$ generated expected output with no evidence of errors (Fig. 2). Mean and standard deviation computed in Matlab were 626.1 ± 4 and 312.6 ± 5 – A1 was $\frac{1}{2}$ of A0.
 - b) Changing $R3$ to $1M\Omega$ changed A0 and A1 to 626.0 ± 3 and 402.1 ± 2.4
 - c) Leaving $R3$ as in b) but grounding A0 $\rightarrow 0 \pm 0$ and 227.8 ± 4.9
 - d) Leaving $R3$ as in b) and c), and measuring $R3$'s voltage on both A0 and A1 in parallel $\rightarrow A0 = 311.8 \pm 1.2$ and $A1 = 310.5 \pm 1.1$

```
...
626    313
626    312
626    313
626    313
626    312
...
```

Figure 2. Arduino output in Serial Monitor was pasted into Matlab.

Discussion: A few other experiments were done, e.g., changing $R1$ and $R2$ to $1M\Omega$, but the above are adequate to understand the underlying phenomena. The Arduino's DC input resistance

is high enough that putting $10\text{k}\Omega$ in series doesn't cause errors. We expected $A1 = \frac{1}{2} A0$ and that's what we measured within 1 ADU (analog-to-digital unit) and within the 1% error rating of the voltage divider resistors. This might protect the input circuits from excess currents if the input voltage exceeds 5V. This is a recipe to protect the Arduino – always put a $10\text{k}\Omega$ resistor in series with A_{in} pins.

- 1) d) tells us that $A0$ and $A1$ differ by 1.3 ADU even though they're measuring the same voltage – so we should consider channel-to-channel variability of $\sim 1\text{--}2\text{ADU}$ as the accuracy limits of this device.
- 2) A $1\text{M}\Omega$ series resistor causes significant errors – $402\text{--}313 = 89\text{ADU}$ and $313\text{--}228 = 85\text{ADU}$, about $87/313 = \pm 27\%$ error. Why is the error sometimes high and sometimes low (by about the same amount)? I think the answer involves the internal 14pF sample and hold capacitor. The error depends on how much the voltage changes between the previous and next measurement. E.g., if $A0$ and $A1$ are at the same voltage, then the capacitance effect is null (result d). But as the voltage differences increase, then the high external resistance doesn't allow the C to charge or discharge before the next reading. If the prior voltage reading was higher, then residual charge on C will make the next reading too high, and conversely, if the prior voltage was lower, then the S/H capacitor won't have time to charge up to the new voltage and the next reading will be low. That's consistent with our results b) and c).
- 3) Theoretically, assuming the quotes we found are true, $10\text{k}\Omega$ in series with 14pF has a [time constant](#)³ of $\tau = 14\text{e-}12 * 1\text{e}4 = .14\mu\text{sec}$, so the $6\mu\text{sec}$ between samples is $6/.14 = 42\tau$ – far more than enough time to settle ($\sim 1\%$ error in 5τ). $R3 = 1\text{M}\Omega$ is 100 times larger, so the $6\mu\text{sec} = .42\tau$, and we'd expect the capacitor to charge to $\sim 1 - \exp(-.42) \sim 34\%$ of the right answer. We got about twice that much (27% error = 63% of the right answer), I think being within a factor of 2 is pretty reassuring.

Conclusions: Input resistance, and more generally, input impedance⁴ (a complex value that includes capacitive resistance), is an important characteristic of a circuit. The high input resistance of the Arduino's analog inputs allows us to add a $10\text{k}\Omega$ resistor in series without causing voltage errors for DC inputs. The series resistor will limit current and protect the Arduino from overvoltages.

Capacitors add significant complexity because their effects depend on their history – how much charge is stored in them from the past. The more resistance in a circuit, the slower the capacitors charge and discharge to equilibrium at DC. With time-varying voltages (AC), there is no static equilibrium, so it's even more challenging. We'll have to wrap our heads around this complicated stuff – and we'll find that complex numbers and Fourier transforms are going to help us *simplify* these characteristic behaviors!

¹ https://en.wikipedia.org/wiki/Thévenin's_theorem

² <https://forum.arduino.cc/index.php?topic=65134.0>

³ https://en.wikipedia.org/wiki/RC_time_constant

⁴ https://en.wikipedia.org/wiki/Electrical_impedance

Appendix: Raw data and analyses

```
>> data = [... % R1=R2=R3=10k
626 313
627 313
627 313
626 313
% about 60 similar lines deleted
626 312
626 313
626 312
626 312
];
>> mean(data)
ans =
    626.0811    312.5946
>> std(data)
ans =
    0.4303    0.4943
>> data = [... % R1 = R2 = 10k, R3 = 1M
626 404
626 404
626 404
% about 60 lines deleted
626 402
626 403
626 402
];
>> mean(data), std(data)
ans =
    625.9848    402.1364
ans =
    0.3278    2.3657
>> data = [... % R1 = R2 = 10k, R3 = 1M, A0 grounded
0 228
0 228
0 229
% about 70 lines deleted
0 229
0 228
0 229
0 229
];
>> mean(data), std(data)
ans =
         0    227.7681
ans =
         0     4.8964
>>
>>
>> data = [... % Same R's, A0 = A1
312 310
% ~150 lines deleted
314 313
310 309
310 309
311 310
];
>> mean(data), std(data)
ans =
    311.7838    310.4775
ans =
    1.1937    1.1371
```